

Grant Lance  
ECE 474 Spring 2024  
Final Project - Microprocessor

This document is broken into two sections- Validation and Unresolved Issues. The first will focus on validating the functionalities that my microprocessor has- ALU/SRU commands, MEMW/MEMR, JMPC/JMPD, and LDI. The second will focus on the issues that I could not resolve before the deadline. Mainly this was the implementation of the stack but also no-op.

### **Validation**

A single test bench that “turns the processor on” is used to demo the code and test its functionality. This is a bit brute force, but allowed me to see how my changes would affect the overall performance of the processor. The main functionalities are split amongst the if\_module and ex\_module. if\_module handles reading the ROM and storing the program count to a stack for JMPS/RETS. ex\_module handles all ALU/SRU operations as well as managing the data memory registers and storage (addressable BRAM). All memory was initialized from the block memory generator in the IP Catalog. This section will have screenshots of the test bench with narration as well as a truth table with expected/actual results. First LDI and ALU/SRU functions will be demonstrated, then MEMW/MEMR, and finally JMPC/JMPD.

#### **ALU/SRU**

The ALU/SRU blocks perform the following functions NAND, NOR, XOR, ADD, ROTL, SLA, SRA, and SRL. In order to be able to demonstrate their functionality LDI is needed alongside: a top module being initiated connecting IF/EX, EX to have ROM reading capabilities, and IF being able to manage a register bank correctly. By testing some commands to load the register banks and perform some operations on them by using the ALU/SRU, all of these functionalities can be validated at once. Figure 1 shows LDI and NOR.

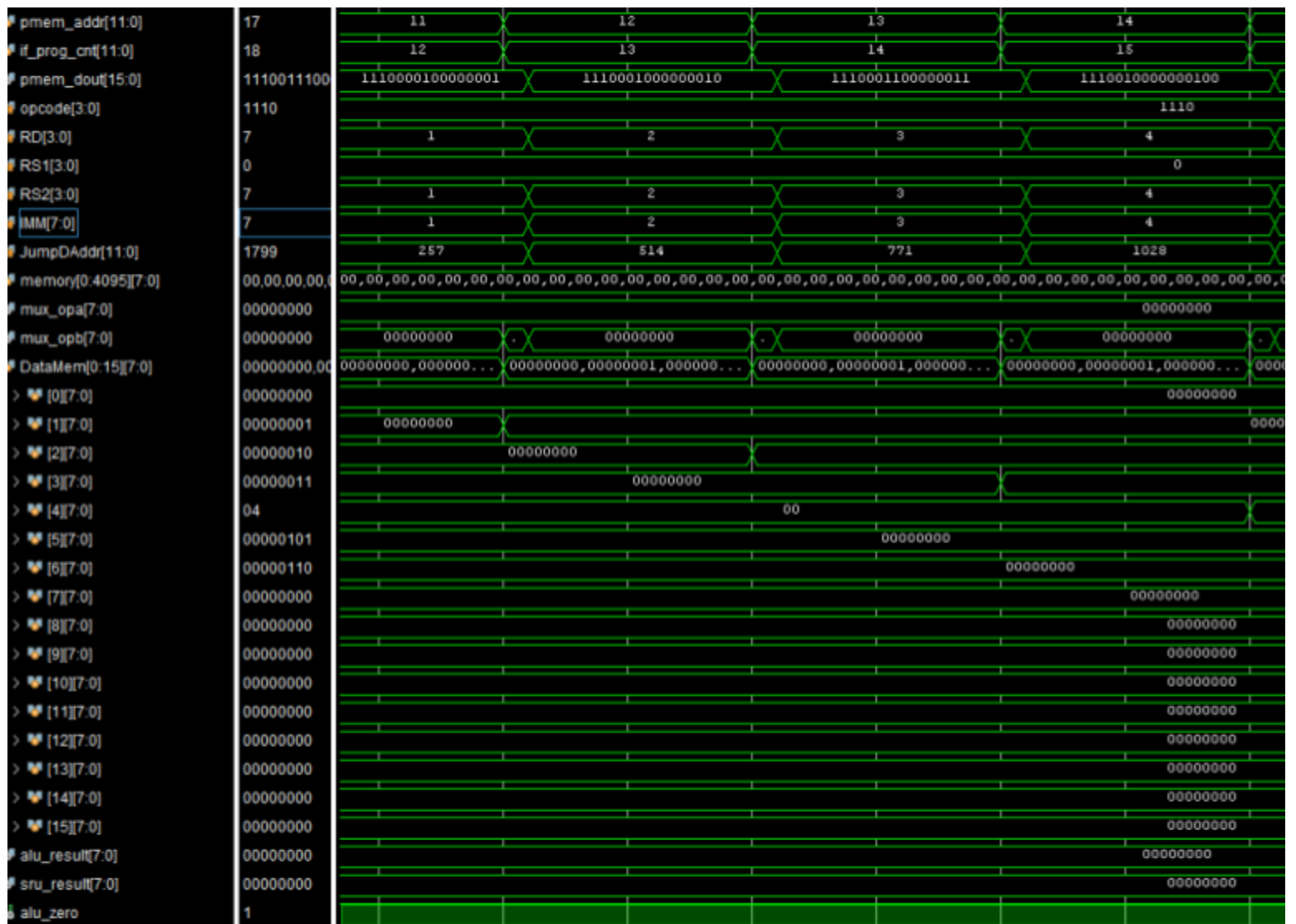


Figure 1: Screenshot of LDI and NOR functionalities

 


Figure 2: Screenshot of LDI and NOR functionalities

Command	OPCODE (4'b)	RD (Decimal)	RS1 (Decimal)	RS2 (Decimal)	IMM/AD DR (Decimal)	Expected Output (Hex/Binary)	Expected Destination (R0-15)	Actual Output (Hex/Binary)	Actual Destination (R0-15)
NOR	0001	0	0	0	n/a	FF	R0	FF	R0
			8'b0	8'b0					
LDI	1110	2	n/a	n/a	2	2	R2	2	R2

NAND	0000	1	1	2	n/a				
			8'b0 0000 001	8'b00 00001 0		FF	R1	FF	R1
XOR	0010	3	3	4	n/a	7	R3	7	R3
			8'b0 0000 011	8'b00 00010 0					
ADD	0011	4	4	5	n/a	9	R4	9	R4
ROTL	0100	5	5	n/a	n/a	8'b0000 1010	R5	8'b00 00101 0	R5
			8'b0 0001 010						
SLA	0101	6	6	n/a	n/a	8'b0000 1100	R6	8'b00 00110 0	R6
			8'b0 0000 110						
SRA	0110	6	6	n/a	n/a	8'b0000 0110	R6	8'b00 00011 0	R6
			8'b0 0001 100						
SRL	0111	6	6	n/a	n/a	8'b0000 0011	R6	8'b00 00001 1	R6
			8'b0 0000 110						

Table 1: SRU/ALU validation

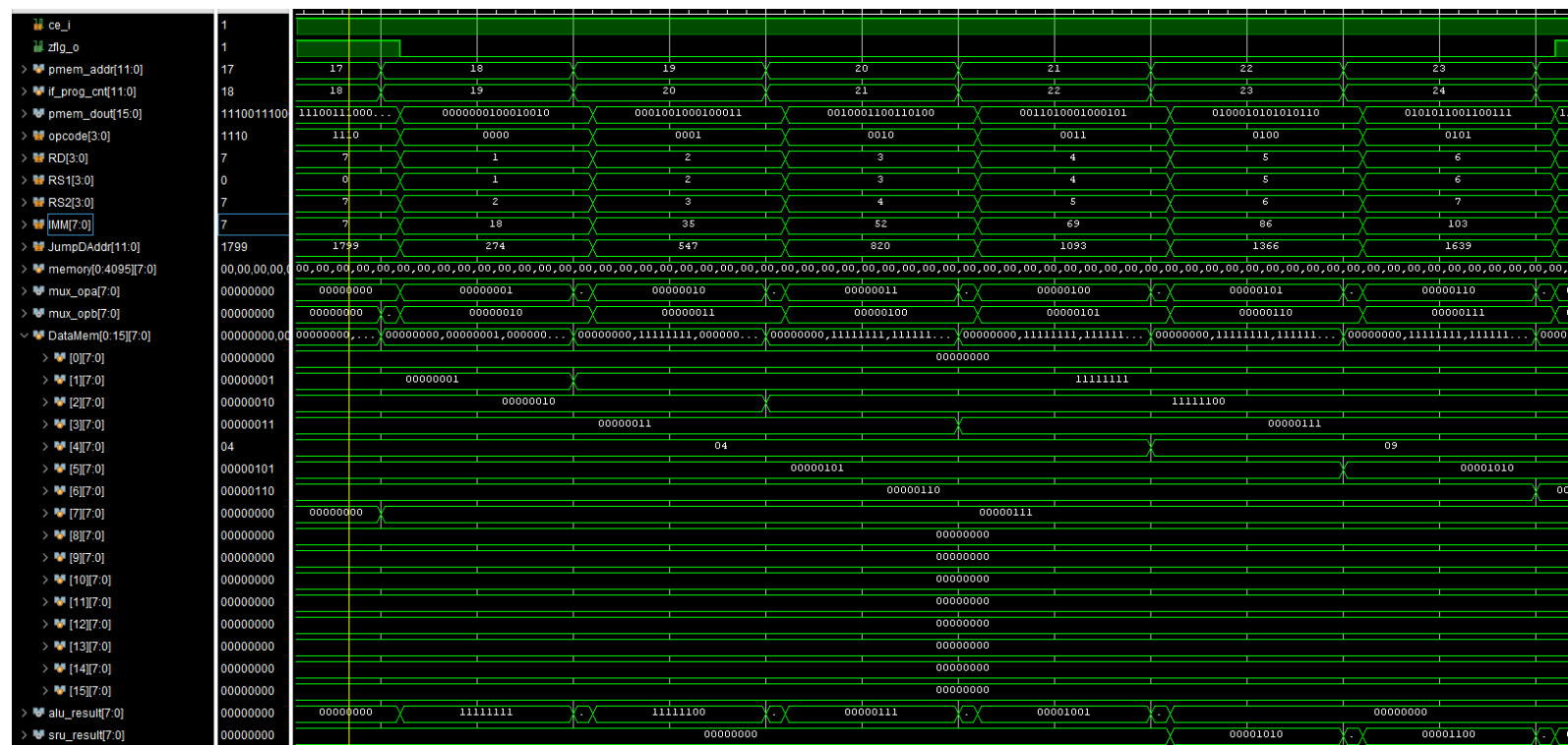


Figure 3: Screenshot of ALU, SLA, and ROTL working

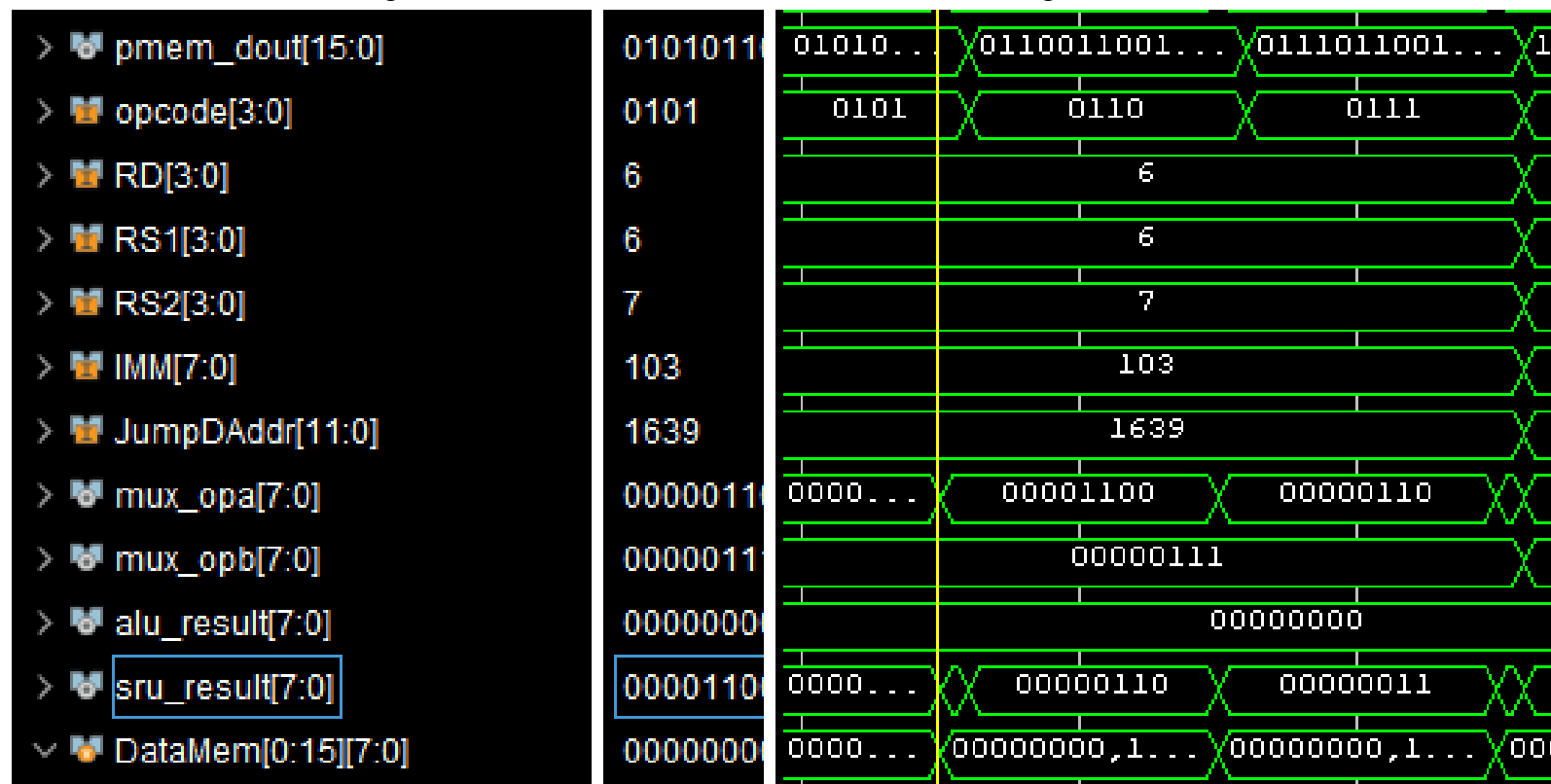


Figure 4: Screenshot of SRA/SRL working

### MEMW/MEMR

MEMW/MEMR is implemented through a BRAM module in EX. EX grabs the relevant data from the requested register and stores it to a memory location specified by the value of another register (MEMW). Also, EX can grab data from storage given an address and a destination register. Below is a screenshot showing two times when MEMW/MEMR was called. In the first instance FC (hex) is stored to memory address 0 (from register 10). It is then read from memory and stored into register 0. This same cycle occurs for F4 further into program memory.

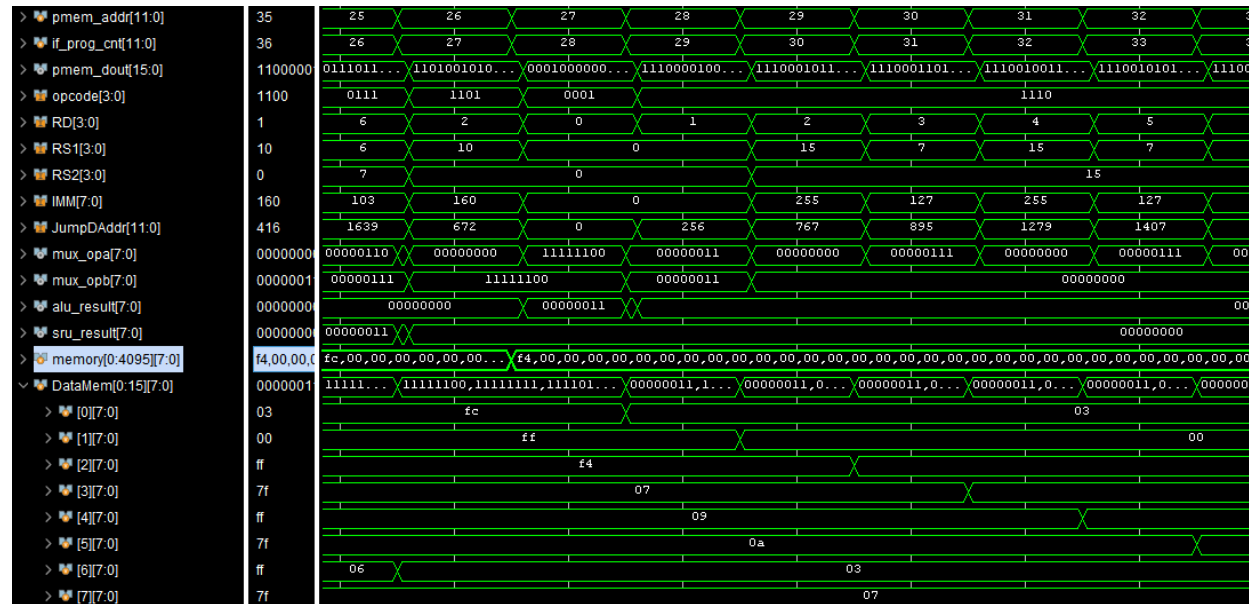


Figure 5: Screenshot of MEMW/MEMR

 


Figure 6: Screenshot of MEMW/MEMR

### JMPD/JMPC

Conditional jump and jump direct both work as expected. The figure below shows an immediate jump to program memory 128 when given the JMPD command with an immediate value of 128.

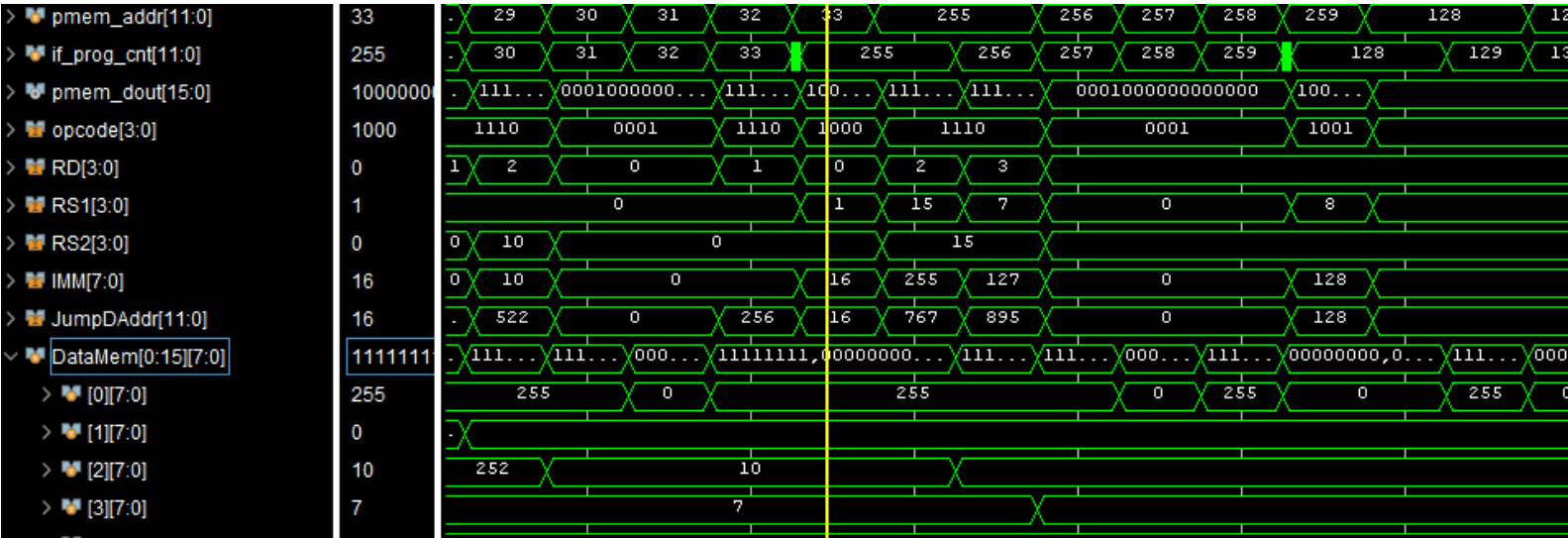


Figure 7: Screenshot of JMPD functioning

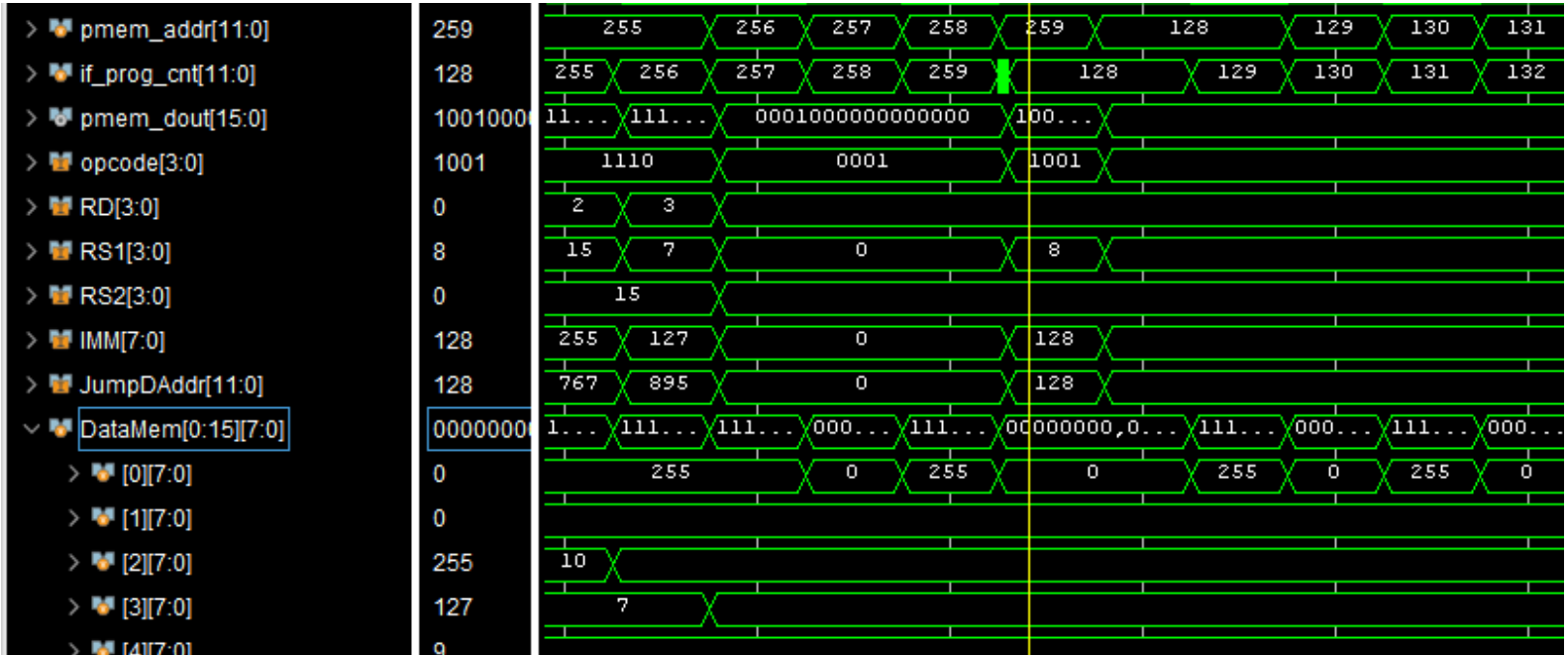


Figure 8: Screenshot of JMPD functioning

### Unresolved Issues

Aside from the issues discussed below, the microprocessor should meet all requirements set by the assignment handout.

### The Stack

[illegible]

### Data Storage

No-Operation

### Synthesis/Clock Speed

Another neglect on my part was that the implementation had to pass synthesis. I did not check this until the end when it was too late. Because of this I also do not know the clock speed of the processor.



## Note Appendix

Data Mem  
16 reg

Prog Mem  
list of Inst

[3:0] [11:0]  
opcode rd/rs1/rs2  
ADDR  
rd/rs1+rs2  
IMM

see ALU flag set to 1  
~~EX~~ ← set done flag

- take opcode  
↳ not IF so

ALU arithmetic  
or

SRU arithmetic

↳ after set ~~ex~~ flag  
done flag 1

on rst  
initialize  
done flag  
↳ 0-1

need to track  
if not received  
or not index  
↳ use index  
pmmr as 1

track when  
reset?  
lower flag when  
prog cnt + 1?

see ~~IF~~ flag set to 1  
get ALU flag

- take opcode  
- ~~take opcode~~  
rd/rs1/rs2 values

- IF opcode

JMPC 4'b1000  
JMOD 4'b1001  
JMPS 4'b1010  
RETS 4'b1011

↳ change PC  
in IF  
accordingly

- else pass  
~~opcode~~ opcode,  
rd, rs1, rs2  
(possibly immediate)  
↳ IMM

to EX  
↳ set ALU flag 1